

## **Laboratory Report 4 Digital Systems**

Module	EE4522. Digital Systems 1
Date	09/02/2023
Lab Number	4
Student Name and id	Mateusz Pluta 22354107

\*Worked with Crian O'Donnel (22346341)

### **Introduction**

In this lab using the base system from Lab 2a, we had to build a new system which has a 7-segment display part in it. The 7-segment display contains seven light-emitting diodes labelled from a to g. Using OR, AND and XOR gates we had to construct the digital system.

### **Procedure**

To construct this board we had to use the base system from lab 2a and then make it so that the 7-segment display creates the numbers 0,1,2 and 3 in this order. To build the 2<sup>nd</sup> part of the system we needed this equipment:

- Another breadboard
- 74HC08 chip
- 74HC14 chip
- 7-segment display
- 330  $\Omega$  resistors
- Extra wires

With these components it was possible to build the circuit using Schematics, photos and wire diagrams. The final design should look like figure 2.

### **Results**

Challenge 4.2 When circuit is finally built, we had to test whether it works. It needed to display 0, 1, 2 and 3 in this order however it didn't work at all of me. I needed to do the Boolean algebra first to (Table 1).

**Table 1:**

x	y	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	1
0	1	1	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0
1	1	0	0	0	0	1	1	0

After completing the truth table I needed to do Boolean algebra to be able to create the wire diagram.

$$A = x' \cdot y$$

$$B = \text{GND}$$

$$C = x \cdot x'$$

$$D = x' \cdot y$$

$$E = y$$

$$F = (x' \cdot y')'$$

$$G = x'$$

As I hadn't made the wire diagram beforehand, the wires were all over the place. So, I made out the wire diagram with the help of technicians. (Figure 1)


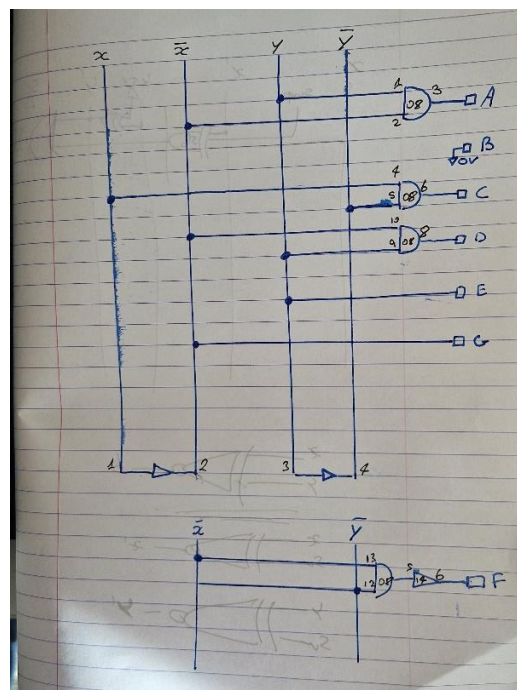


Figure 1 Wire diagram to make 0,1,2,3.

 Challenge 4.1 I was then finally able to complete the circuit with it properly working as expected. (Figure 2,3,4,5)



Figures 2,3,4 and 5 displaying the numbers shown on the board

Challenge 4.3 – Test or fail verification table.

**Table 2**

7-segment display outputs	Pass or fail
0	Pass
1	Pass
2	Pass
3	Pass

Challenge 4.4 We had to download the simulation model from sulis and run the simulator. The Simetrix model looks like figure 6.

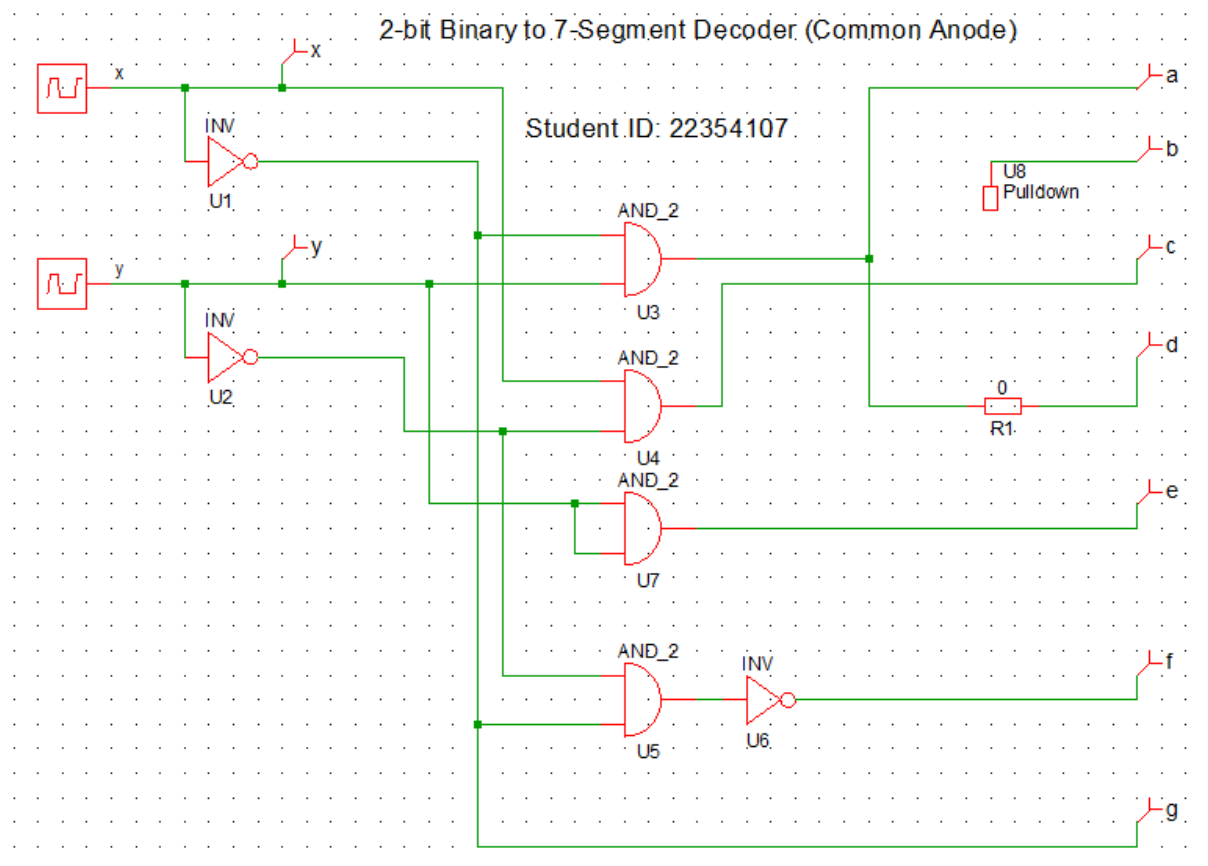


Figure 6 Simetrix model of the circuit

When the simulation is run, we get from x, y and from a to g plots (Figure 7). As we can see each represent a binary path just like we can see in Table 1. When the line is at the bottom it means its at 0 and when the line is at the top it means its 1.

 


Figure 7 Plots of x, y and a to g.



Challenge 4.5:- We had to build an advanced circuit using an XOR gate (74HC86) and instead of the 7-segment display, displaying 0, 1, 2, 3. We needed it to display A, b, c, d as seen in figures 8,9,10 and 11.

 


Figure 8,9,10 and 11 Pictures of advanced circuit

Once again, I needed to create another wire diagram and algebra to be able to build the circuit.

$$a = (x' \cdot y')'$$

$$b = x \cdot y$$

$$c = x \cdot y'$$

$$d = x' \cdot y'$$

$$e = \text{GND}$$

$$f = x$$

$$g = \text{GND}$$

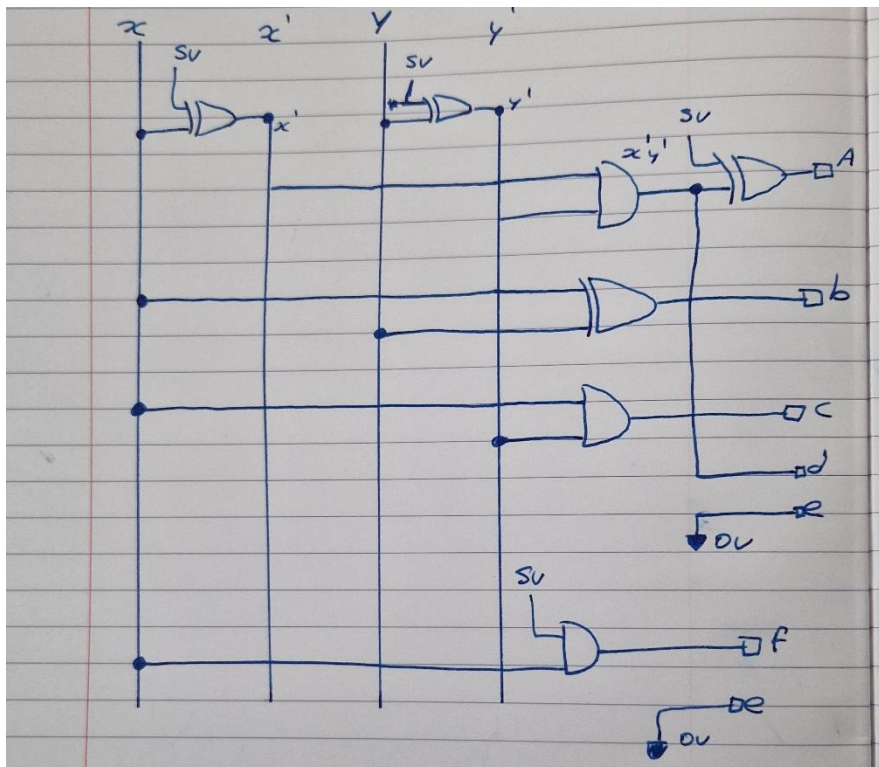


Figure 12 The wire diagram for advanced circuit

I have successfully been able to construct the circuit and worked perfectly when I tested it. I had trouble understanding the "b" but the technicians assisted me greatly.

**Table 3**

7-segment display outputs	Pass or fail
A	Pass
b	Pass
c	Pass
d	Pass

## **Conclusion**

In conclusion I was able to complete both circuits and understand how XOR, OR and AND gates work which was complicated at first as I didn't understand the algebra however the technicians assisted me with it. I was also able to complete every challenge without much trouble.

Declaration of authorship: "I confirm that this lab report, submitted for assessment, is my own original work".